



University of British Columbia
Electrical and Computer Engineering
ELEC291/ELEC292

Project 1 – Reflow Oven Controller

Dr. Jesús Calviño-Fraga P.Eng.
Department of Electrical and Computer Engineering, UBC
Office: KAIS 3024
E-mail: jesusc@ece.ubc.ca
Phone: (604)-827-5387

January 31, 2020

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

1

Objectives

- Learn about reflow soldering thermal profiles.
- Understand the steps used in the assembling of PCBs with SMT components.
- Understand the components of a reflow oven controller.
- Measure temperature using a thermocouple.
- Control and AC load using a Solid State Relay.


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

2

Reflow Soldering Profile

http://en.wikipedia.org/wiki/Reflow_soldering

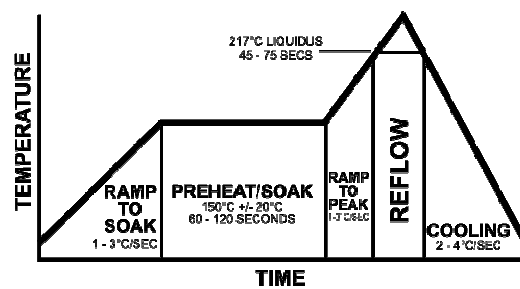


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

3

Solder Paste Profile (SAC305)

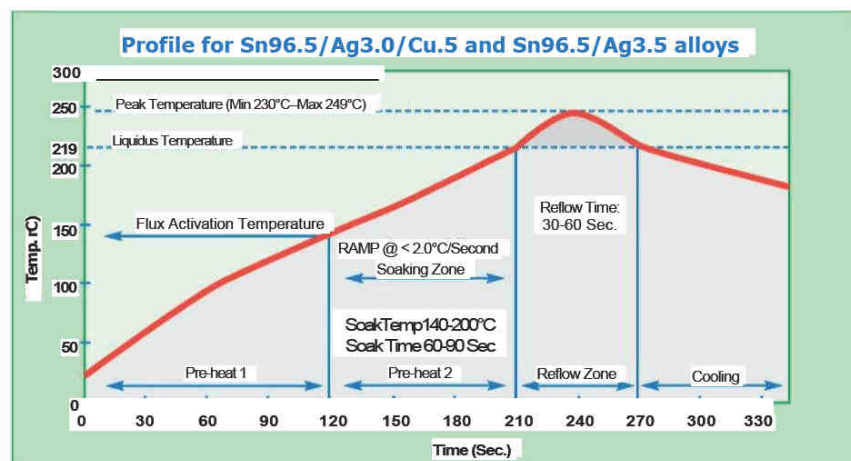


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

4

SMT Component Thermal Profile

Figure is from LTC6655 datasheet

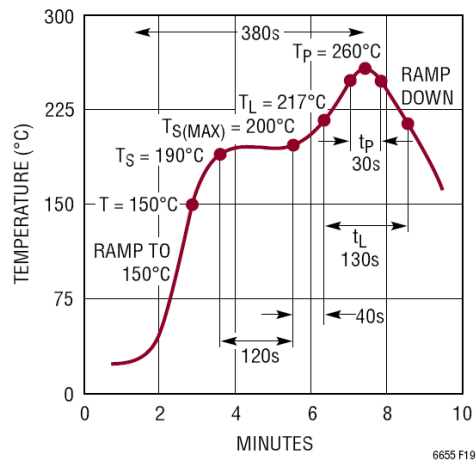


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

5

My tests thermal profile

Current Oven Temperature: 59.0

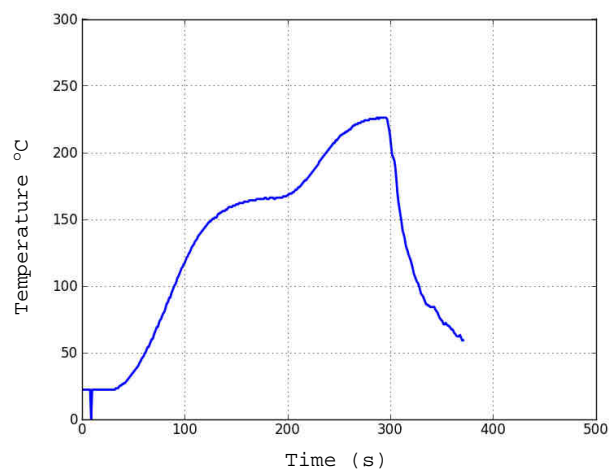

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

6

Warnings:

- Don't let your reflow time be more than 45s or the silk screen may darken.
- Don't let your reflow max temperature climb over 235 °C or your PCB may burn: lots of smelly smoke!

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

7

PCB Burnt in Reflow Oven



Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

8

Steps Assembling a PCB with SMT components.

- Step 1: Apply solder paste to the PCB. You will use a Mylar stencil. **(I personally believe this is the most critical step in the whole process!)**
- Step 2: Place the SMT components into the PCB.
- Step 3: Reflow soldering. You will be using a toaster oven with a controller of your own design.
- Step 4: Hand soldering of TH (thru hole) components.

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

9

Steps Assembling a PCB with SMT components.

- Video 1 shows how I applied solder paste and placed the components by hand using tweezers.
http://courses.ece.ubc.ca/281/2017/Paste_and_Components_Slow.mp4
http://courses.ece.ubc.ca/281/2017/Paste_and_Components_Fast.mp4
- Video 2 Shows how I cleaned the stencil
<http://courses.ece.ubc.ca/281/2017/Cleaning.mp4>
- Video 3 shows how I reflow soldered the SMT components using a toaster oven.
<http://courses.ece.ubc.ca/281/2017/Reflow.mp4>
- Video 4 shows how to remove a solder bridge
http://courses.ece.ubc.ca/281/2017/Bridge_removal_horizontal.mp4
- Video 5 shows how I soldered the TH components.
http://courses.ece.ubc.ca/281/2017/Thru_hole.mp4

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

10

Mastering the Tweezers and Loupe, Step 1: find tools and materials




Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

11

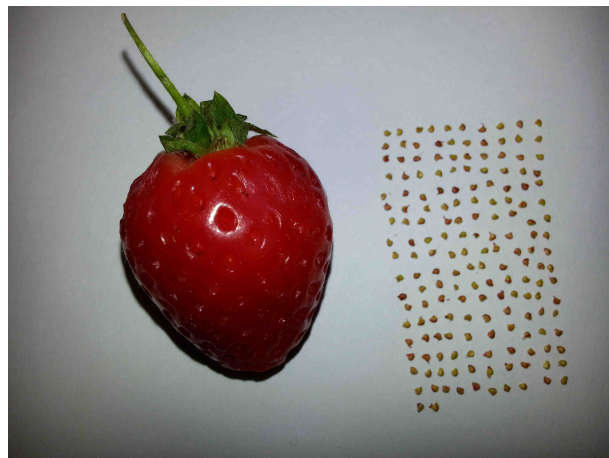Mastering the Tweezers and Loupe, Step 2: remove seeds!




172 seeds!

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

12

Oven Controller Typical Block Diagram

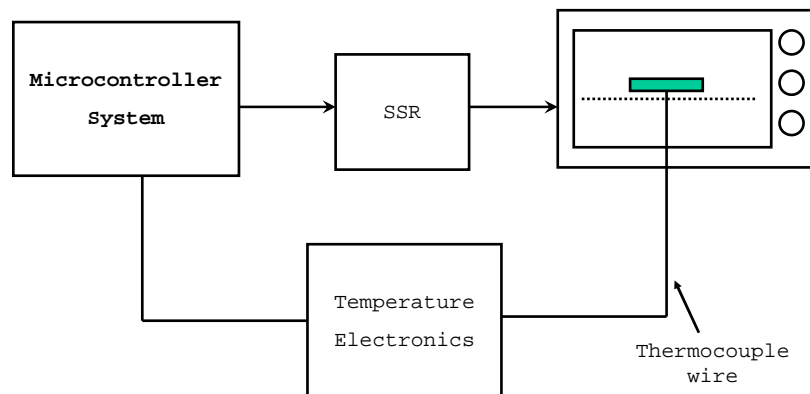

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

13

Microcontroller Requirements

- Must not be an AT89LP51RC2 (or any other member of the AT89LP family from Atmel/Microchip)
- Provided: EECE281 board. Uses the P89LPC9351 microcontroller. 8051 compatible.
- EFM8: Assemble this 8051 microcontroller boards as part of project 1.

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

14

Other Requirements

- Selectable reflow profile parameters.
- Display of temperature (s), running time, and reflow process current state using an LCD.
- Talk feedback: temperature, current state, warnings, errors, instructions, etc.
- Start/Stop pushbutton.
- Temperature strip chart plot using the serial port of the system and a personal computer.

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

15

K-Type Thermocouple

- Has two wires: Yellow (+) and Red (-).
- About $41 \mu\text{V}/^{\circ}\text{C}$. You'll need an amplifier!
- Very accurate conversion table provided by the National Institute of Standards and Technology (USA):


http://srdata.nist.gov/its90/download/type_k.tab

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

16

Using a K-type Thermocouple

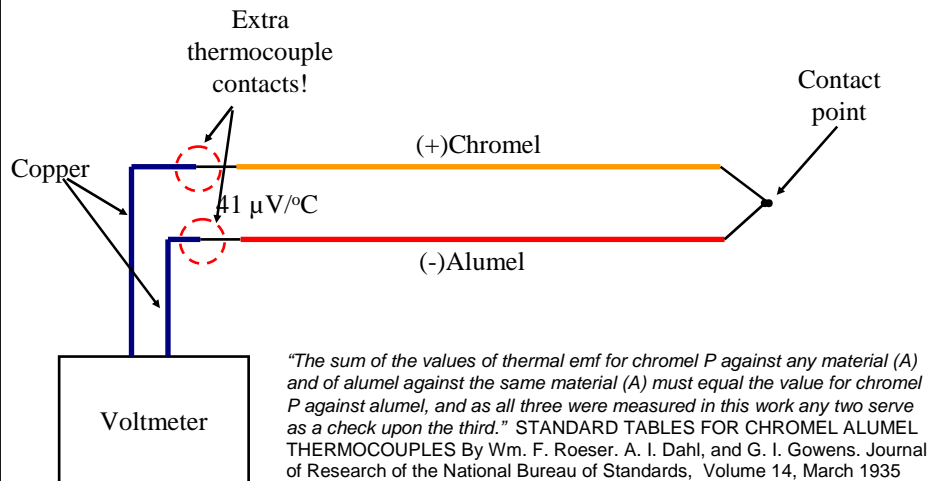


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

17

Using a K-type Thermocouple

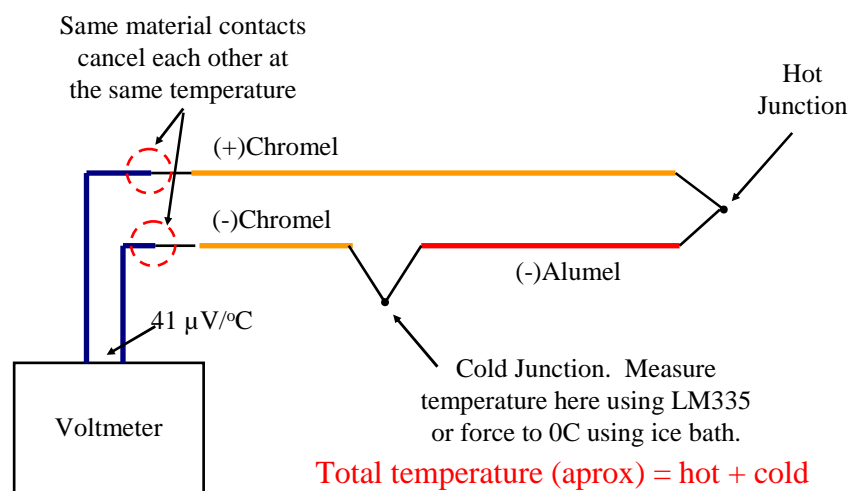

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

18

Testing a K-Type Thermocouple in the Laboratory. You'll need:


- Thermocouple wire: included in project kit.
- Voltmeter with micro-volt resolution: Fluke 45 or Tektronix DM4020.
- Ambient temperature in the lab. Most of the time between 20C and 24C. If not measured, use 22C. Or use your LM335!
- USB to serial adapter attached to the multimeter to connect a computer. Some already connected to the multimeter close to the toaster ovens.
- Python 3.x.x, 'kconvert.py', and 'Multimeter_Temp.pyw' (you need both files!)

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

19

Testing a K-Type Thermocouple in the Laboratory: Setup

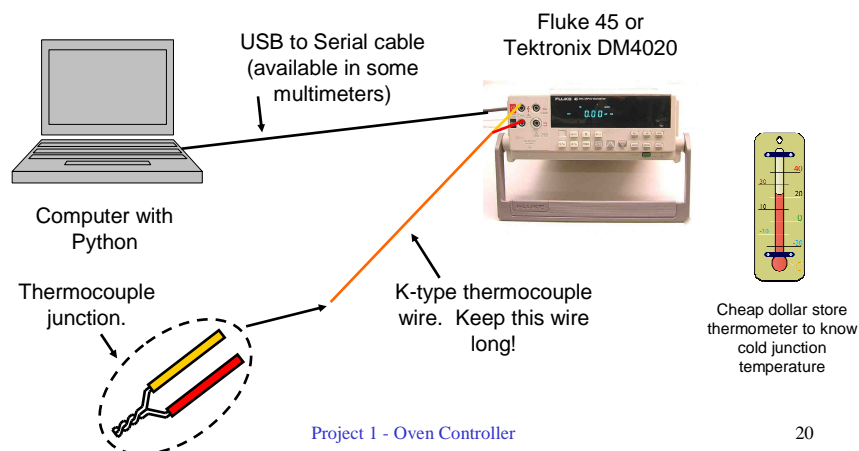


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

20

Run 'Multimeter_Temp.pyw'

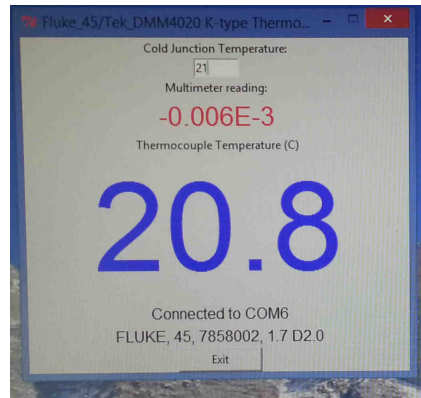


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

21

Run 'Multimeter_Temp.pyw'

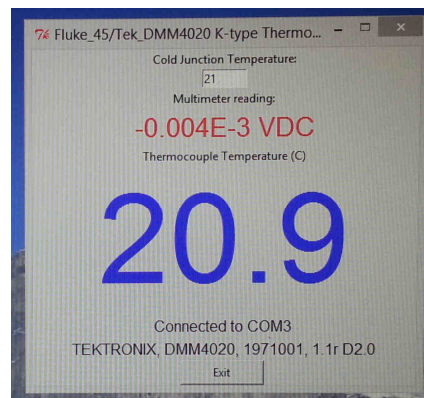


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

22

Amplifying the Thermocouple Voltage

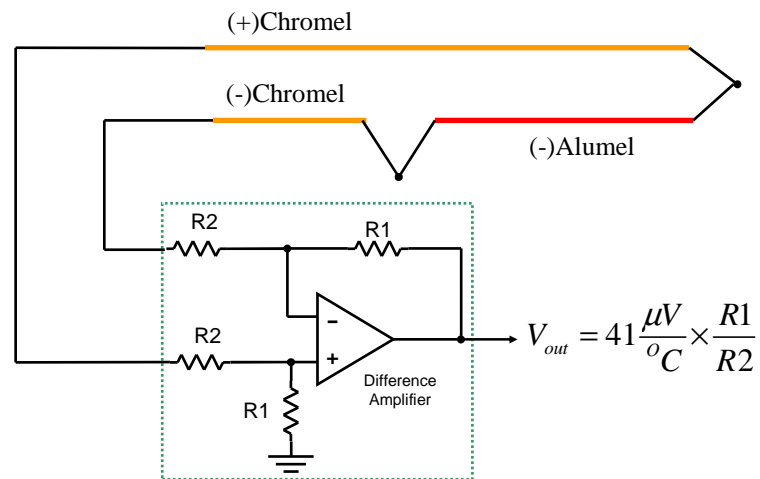


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

23

Making the Junctions

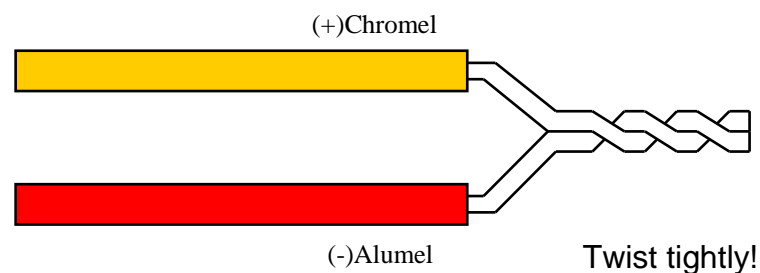


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

24

Good Reference: Microchip AN844

FIGURE 4: HOT OR COLD ONLY MEASUREMENT

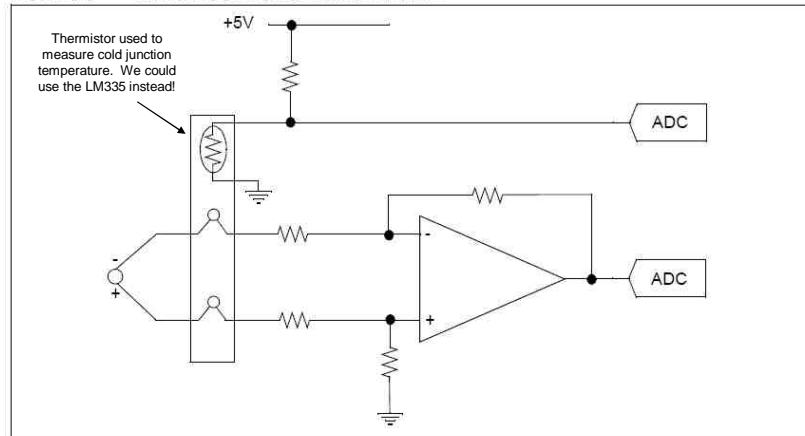

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

25

Opamp

- Must have very small input offset voltage, or offset null circuit.
- The OP07 provided in the microcontroller kit has a typical offset voltage of $50\mu\text{V}$. Sometimes is $200\mu\text{V}$! The offset can be null using a potentiometer.
- The OP07 needs dual power supplies, for example $+5\text{V}$ and -5V . LMC7660 (or equivalent, included in the microcontroller kit) can be used to produce -5V from $+5\text{V}$.
- Choose the gain carefully! The OP07 will saturate at a voltage below $+V$.

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

26

Opamp

Data Sheet

OP07

FEATURES

Low V_{OS} : 75 μV maximum
 Low V_{OS} drift: 1.3 $\mu V/^{\circ}C$ maximum
 Ultrastable vs. time: 1.5 μV per month maximum
 Low noise: 0.6 μV p-p maximum
 Wide input voltage range: $\pm 14 V$ typical
 Wide supply voltage range: $\pm 3 V$ to $\pm 18 V$
 125 $^{\circ}C$ temperature-tested dice

APPLICATIONS

Wireless base station control circuits
 Optical network control circuits
 Instrumentation
 Sensors and controls
 Thermocouples
 Resistor thermal detectors (RTDs)
 Strain bridges
 Shunt current measurements
 Precision filters

PIN CONFIGURATION

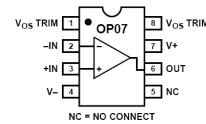


Figure 1.

The wide input voltage range of $\pm 13 V$ minimum combined with a high CMRR of 106 dB (OP07E) and high input impedance provide high accuracy in the noninverting circuit configuration. Excellent linearity and gain accuracy can be maintained even at high closed-loop gains. Stability of offsets and gain with time or variations in temperature is excellent. The accuracy and stability of the OP07, even at high gain, combined with the freedom from external nulling have made the OP07 an industry standard for instrumentation applications.

Project 1 - Oven Controller

27

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Optional Offset Nulling

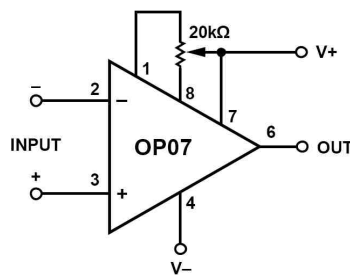


Figure 28. Optional Offset Nulling Circuit

Project 1 - Oven Controller

28

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Opamp needs $\pm 5V$

www.ti.com

SNOSBZ9C – APRIL 1997 – REVISED APRIL 2013

LMC7660 Switched Capacitor Voltage Converter

Check for Samples: [LMC7660](#)

FEATURES

- Operation Over Full Temperature and Voltage Range without an External Diode
- Low Supply Current, 200 μA Max
- Pin-for-pin Replacement for the 7660
- Wide Operating Range 1.5V to 10V
- 97% Voltage Conversion Efficiency
- 95% Power Conversion Efficiency
- Easy to Use, Only 2 External Components
- Extended Temperature Range

DESCRIPTION

The LMC7660 is a CMOS voltage converter capable of converting a positive voltage in the range of +1.5V to +10V to the corresponding negative voltage of -1.5V to -10V. The LMC7660 is a pin-for-pin replacement for the industry-standard 7660. The converter features: operation over full temperature and voltage range without need for an external diode, low quiescent current, and high power efficiency.


The LMC7660 uses its built-in oscillator to switch 4 power MOS switches and charge two inexpensive electrolytic capacitors.

Project 1 - Oven Controller

29

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

LMC7660

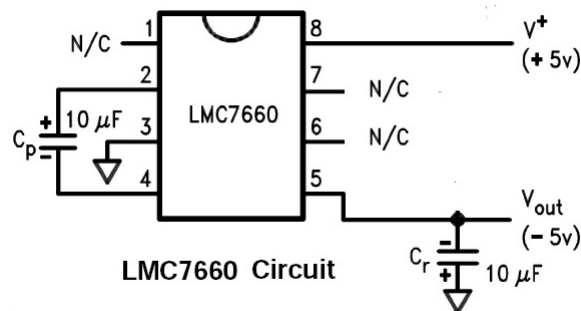

Project 1 - Oven Controller

30

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Temperature Validation Data

- Use the lab multimeter to validate your controller temperature measurements.
- Max acceptable error $\pm 3^{\circ}\text{C}$ for the range 25°C to 235°C .
- You must include the procedure and the data in the project report. Have it handy for the project demonstration!

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

31

Example of controller temperature differences (compared to Fluke 45)

20C	????	????	????	+0.7	+0.8	+1.1	+1.4	+1.4	+1.2	+1.3
30C	+1.3	+1.6	+1.0	+0.0	+0.2	+0.0	+0.3	+0.4	+0.9	+0.4
40C	+0.2	+0.2	+0.2	????	+0.3	+0.0	+0.1	+0.1	+0.2	+0.1
50C	+0.0	+0.1	+0.0	-0.3	+0.2	+0.5	+0.5	+0.4	+0.6	+0.7
60C	+0.6	+0.9	+0.7	+0.7	+0.7	+0.7	+0.3	+0.7	+0.2	+0.4
70C	+0.3	+0.1	+0.4	+0.2	+0.8	+0.4	+0.6	+0.5	+0.2	+0.4
80C	+0.0	+0.1	+0.1	+0.3	+0.1	+0.2	+0.0	-0.1	-0.2	+0.6
90C	+0.8	+0.3	-0.7	+0.0	+0.4	+0.1	-0.2	+0.0	+0.0	-0.9
100C	-0.5	-0.2	-0.1	-0.3	-0.5	+0.1	+0.4	+0.1	+0.6	+0.3
110C	????	+0.4	-0.4	+0.2	+0.9	+0.8	-0.3	-0.2	+0.4	-0.6
120C	+0.5	-0.2	+1.7	+0.5	+0.1	+0.3	-0.2	-0.1	-0.1	+0.3
130C	+0.2	+0.9	+0.6	+0.3	-0.6	+0.2	+0.6	+0.5	+0.6	+1.3
140C	+1.0	+0.6	+1.2	+1.3	+0.5	+0.4	+0.9	+0.3	+0.5	+0.6
150C	+0.0	+0.8	+0.4	+0.4	+1.1	+1.2	+1.0	+1.3	+1.2	+1.1
160C	+1.0	+1.7	+1.0	+1.2	+0.3	+0.4	+0.4	+0.3	+1.1	+0.6
170C	+0.6	+1.1	+1.0	+0.9	+0.8	+0.6	+0.6	+0.8	+0.9	+0.9
180C	+0.7	+0.6	+0.6	????	+0.3	+0.8	+1.5	+1.5	+1.5	+1.2
190C	+1.0	+0.5	+1.1	+0.6	+0.5	+0.5	+0.7	+0.6	+0.3	+0.4
200C	+0.9	+0.8	+1.4	+0.6	+0.9	+0.8	+0.3	+0.4	+0.3	+0.9
210C	+0.4	+1.3	+0.3	+0.7	+0.7	+0.4	+0.5	+0.8	+0.9	+0.5
220C	+0.9	+0.6	+0.8	+0.9	????	+0.4	+0.5	+0.7	+0.5	+0.4
230C	+0.7	+0.8	+0.2	+0.4	+0.4	+0.9	+0.9	+0.8	+0.8	????

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

32

Sources of Error

- The amplifier has too much offset. Solution 1: null the offset using a potentiometer. Solution 2: use an ultra low offset op-amp (for example OP177; expensive!)
- Amplifier resistors mismatch resulting in incorrect gain. Solution 1: use the lab multimeter to select resistor that match. Solution 2: buy 1% or 0.1% tolerance resistors (may be expensive!)
- Incorrect cold junction temperature. Solution 1: adjust the output of the LM335 using a potentiometer. You may need an external thermometer or an ice bath to perform a “one point” calibration of the LM335. Solution 2: buy a low error temperature sensor (may be expensive!)
- Conversion from ADC to voltage gives inaccurate values. Solution 1: measure the “Vref” pin of the ADC using the lab multimeter and use that value in your firmware calculations. Solution 2: buy and use a voltage reference IC (expensive!). Solution 3: use LED voltage to calculate VREF.
- The conversion from voltage to temperature introduces unacceptable errors. Solution 1: tune up your calculations. Solution 2: use a look-up table.

Project 1 - Oven Controller

33

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Testing Your Controller with Paper!



Paper measures
7cm x 2cm


Paper shows reflow
temperature and
time

Project 1 - Oven Controller

34

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

Checking Oven Hot/Cold Spots

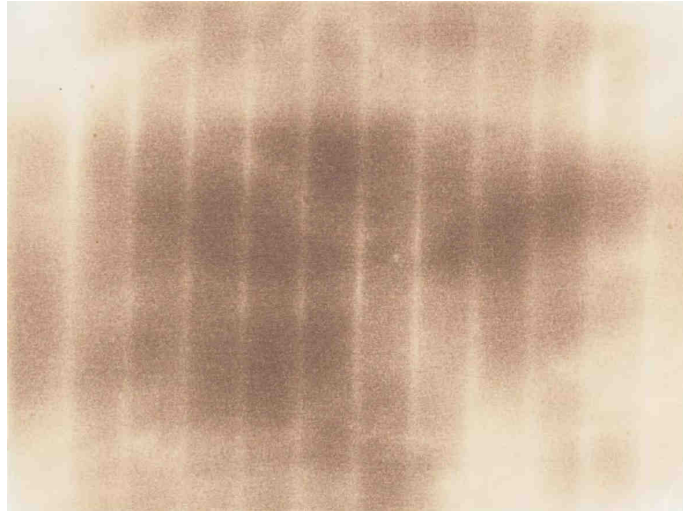

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

35

Professionalism

- The first tenant of the code of ethics of professional engineers reads¹: “*Hold paramount the safety, health and welfare of the public, the protection of the environment and promote health and safety within the workplace*”.
- In the spirit of the above tenant, your reflow oven controller must be designed, built, and tested accordingly.
- Please include in your report any features, designs, procedures, as well as other activities you used to accomplish this requirement.


¹ <https://www.apeg.bc.ca/getmedia/e8d858f5-e175-4536-8834-34a383671c13/APEGBC-Code-of-Ethics.pdf.aspx>

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

36

SSR box block diagram

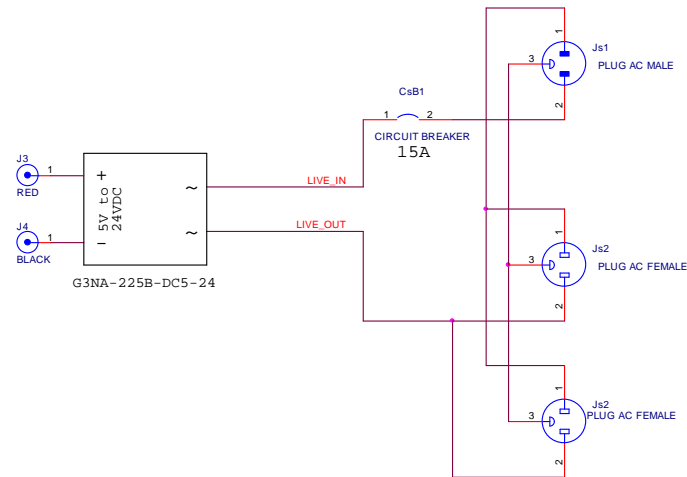


Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

37

Using a I/O pin to Control SSR Box

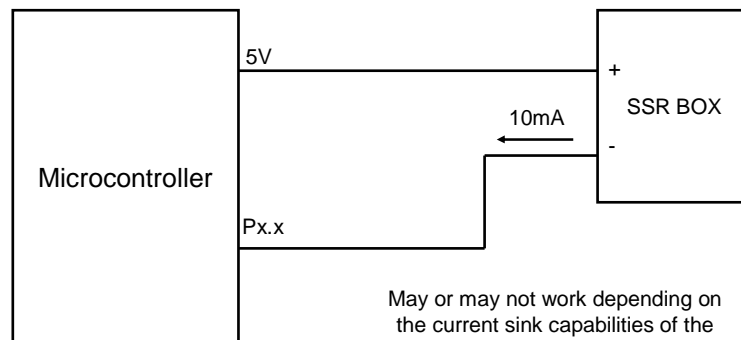


May or may not work depending on the current sink capabilities of the pin/microcontroller used

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

38

Using a Transistor (more reliable)

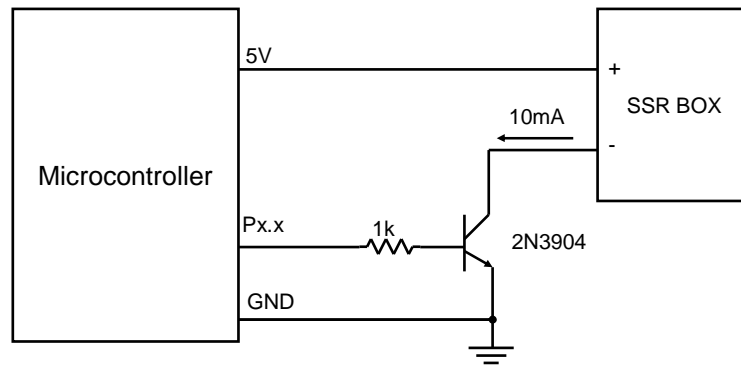

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

39

Using the SSR box

- Connect a power cord cable to the male AC connector. The power cord cable must be rated for the type of load to be connected. If the SSR box would be used to power a 1500W toaster oven, the power cord cable must be rated for at least 13A.
- Connect the AC load to one of the available AC plugs.
- Apply a DC voltage from 5V to 24V to the control banana plugs.
- We got the SSR box CSA approved!

Project 1 - Oven Controller

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

40

Using the SSR box

- Do not operate the SSR box for more than 30 minutes at the maximum rated current of 15A.
- The SSR box is designed for resistive loads only. Do not plug inductive loads (such as motors) to the SSR box.
- Do not operate the SSR box if the ambient temperature is above 40°C.
- The SSR box may become warm to the touch after using it for several minutes at maximum rated capacity. If you suspect that the case temperature is over 40°C discontinue using the SSR box immediately.
- Only apply a DC voltage from 5V to 24V to the control pins. Do not apply negative DC voltages of ANY magnitude.
- Do not disassemble the SSR box.
- If the protection breaker is tripped, find and correct the cause of the fault before resetting the breaker to normal operating mode.

Project 1 - Oven Controller

41

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.

LPCM sound output

- Zip file available on Canvas ('LPCM_Sound_with_P89LPC9351.zip') on how to setup the ICs (25Q32 flash memory, and LM386 audio amplifier) with the P89LPC9351 microcontroller (check for file "Adding Wav Sound to a P89LPC9351.pdf").
- Instruction on how to generate a WAV file.
- Program to run in the computer and P89LPC9351 to store WAV file in 25Q32.
- Playback example for P89LPC9351.

Project 1 - Oven Controller

42

© Jesús Calviño-Fraga, 2009-2020. Not to be copied, used, or revised without explicit written permission from the copyright owner.